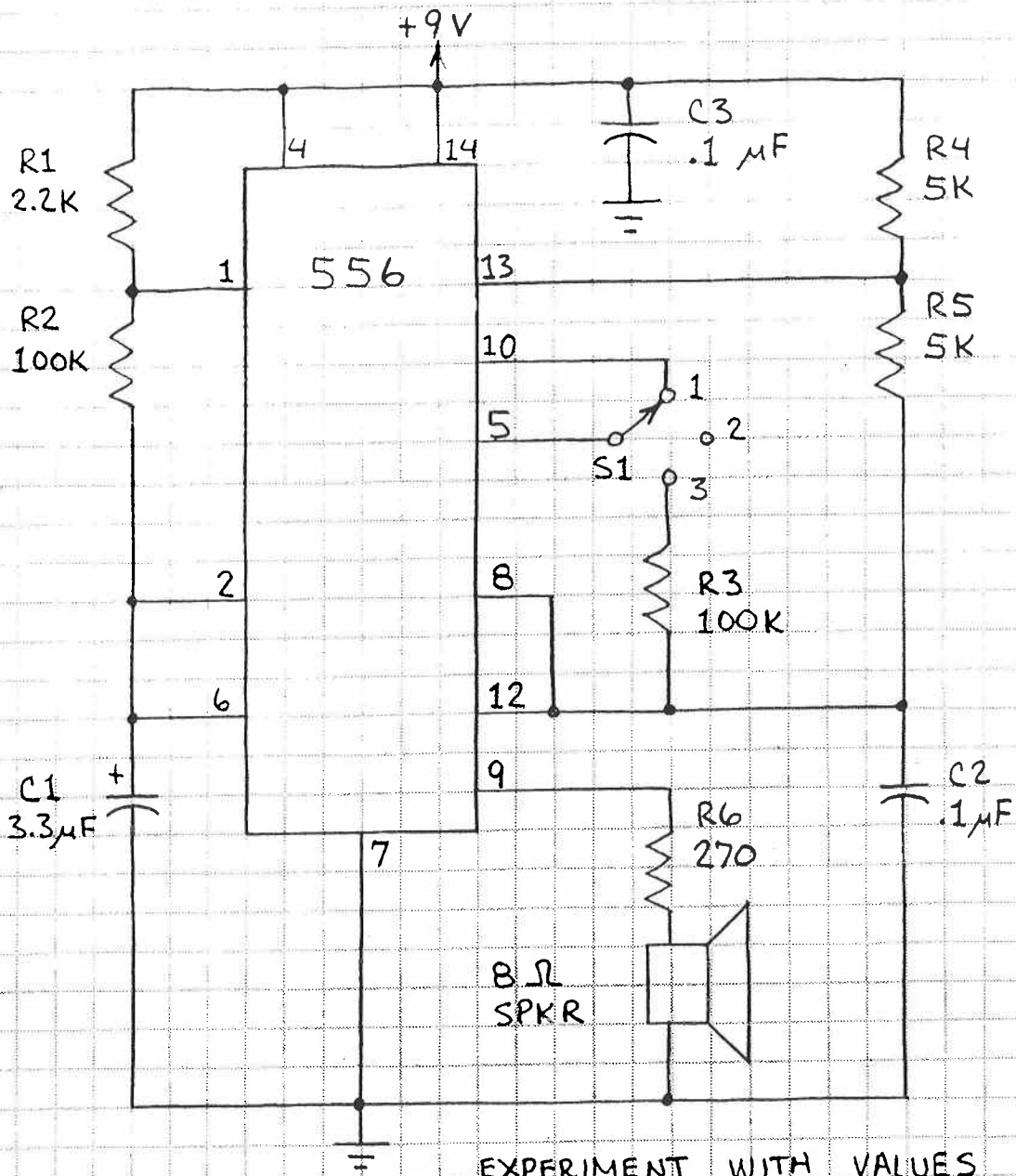


3-STATE TONE GENERATOR



EXPERIMENT WITH VALUES OF R1, C1, R4 AND C2.

S1 (CENTER OFF):

1 - TONE BURST 

2 - STEADY TONE 

3 - TWO-TONE 