

TOY ORGAN

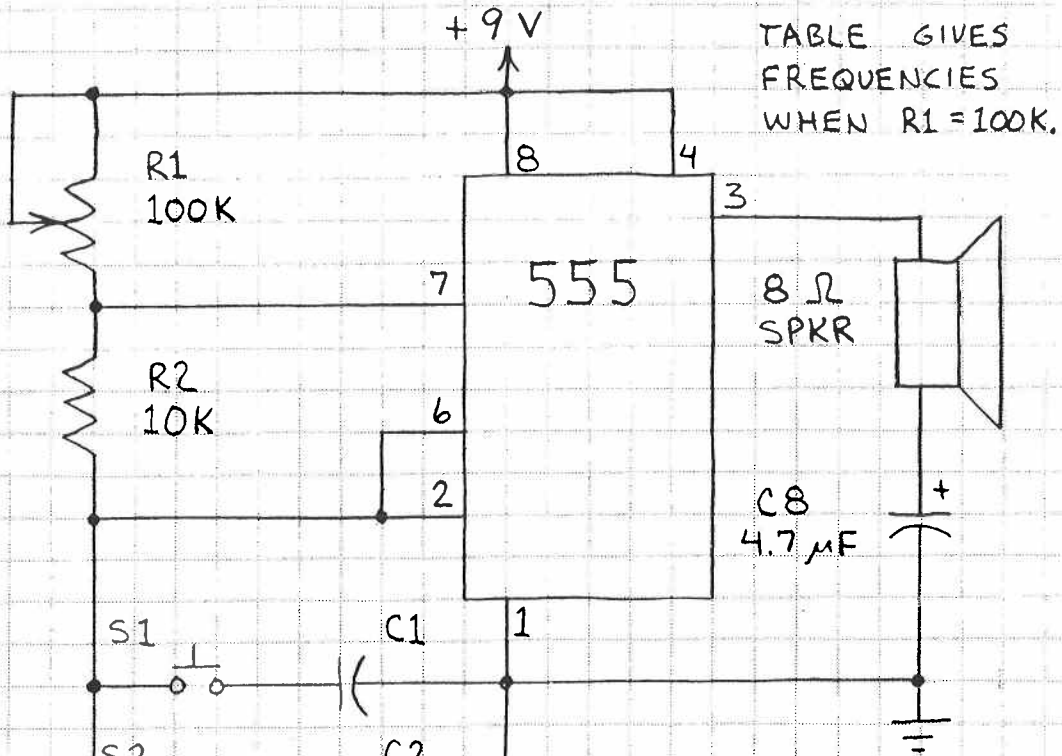


TABLE GIVES
FREQUENCIES
WHEN R1 = 100K.

INSERT 1K POTENTIOMETER
BETWEEN C8 AND SPKR
TO CONTROL VOLUME.

C (μF)	FREQUENCY (Hz)
.22	52
.15	78
.1	111
.068	170
.047	230
.033	348
.022	490
.015	718
.01	1,173
.0068	1,670
.0047	2,240
.0033	3,252
.0022	4,671
.0015	6,336
.001	9,237

Y OK TO ADD
ADDITIONAL
CAPACITORS.